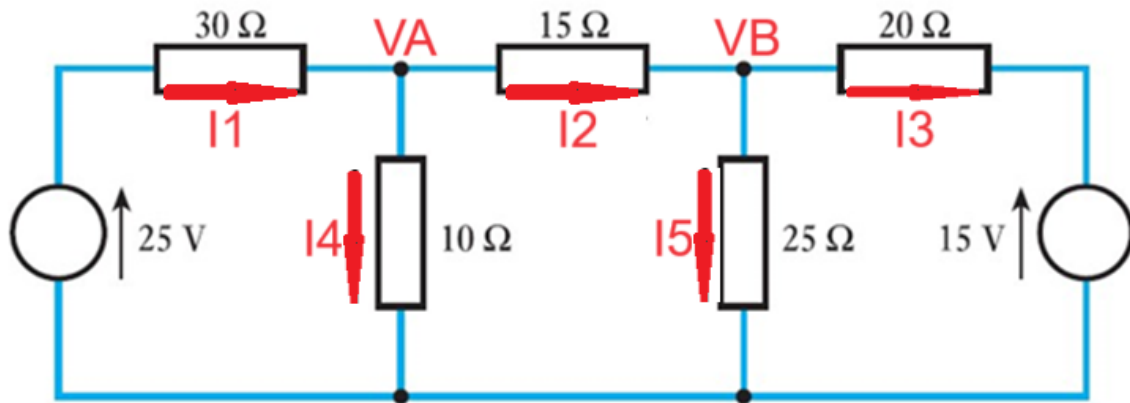


Coursework 1

The coursework is finished by Jiale Fu (2543035) and Zijun Liu (2543336) in Transportation D2201.

Q1



Q1-1

Let us suppose that the current pass through the five resistors is I_1, I_2, I_3, I_4, I_5 , and the position of the upper joints are V_A, V_B .

We can get:

$$I_1 = I_4 + I_2$$

$$I_2 = I_5 + I_3$$

$$I_1 = \frac{25 - V_A}{30}$$

$$I_4 = \frac{V_A}{10}$$

$$I_2 = \frac{V_A - V_B}{15}$$

$$I_5 = \frac{V_B}{25}$$

$$I_3 = \frac{V_B - 15}{20}$$

In this case, we can get:

$$30I_4 + 30I_5 + 30I_3 + V_A = 25$$

$$10I_4 - V_A = 0$$

$$15I_5 + 15I_3 - V_A + V_B = 0$$

$$25I_5 - V_B = 0$$

$$20I_3 - V_B = -15$$

Using the following python code to solve the equations:

```
import numpy as np

A = np.array([[30, 30, 30, 1, 0],
              [10, 0, 0, -1, 0],
              [0, 15, 15, -1, 1],
              [0, 25, 0, 0, -1],
              [0, 0, 20, 0, -1]])
b = np.array([25, 0, 0, 0, -15])

x = np.linalg.solve(A, b)

print("solution is:")
print(x)
```

The solution is:

[0.6714876 0.30578512 -0.3677686 6.71487603 7.6446281]

Which means that:

$$I_1 = 0.6095A$$

$$I_2 = -0.0620A$$

$$I_3 = -0.3678A$$

$$I_4 = 0.6715A$$

$$I_5 = 0.3058A$$

$$V_A = 6.7149V$$

$$V_B = 7.6446V$$

So, the voltage drops are:

$$V_{D1} = 25V - V_A = 18.2851V$$


$$V_{D2} = V_A - V_B = -0.9297V$$

$$V_{D3} = V_B - 15 = -7.3554V$$


$$V_{D4} = V_A = -6.7149V$$


$$V_{D5} = V_B = 7.6446V$$

Q1-2

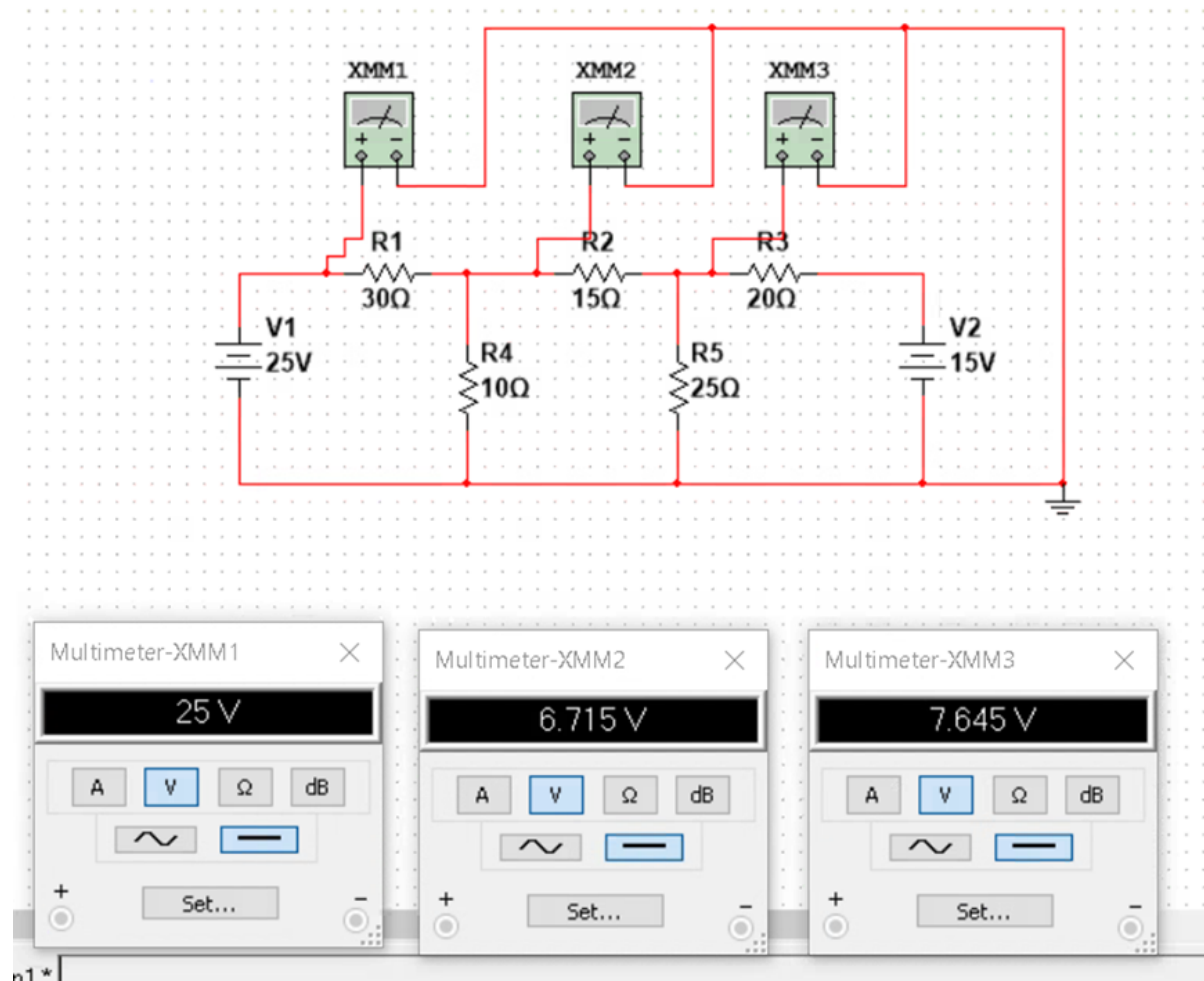

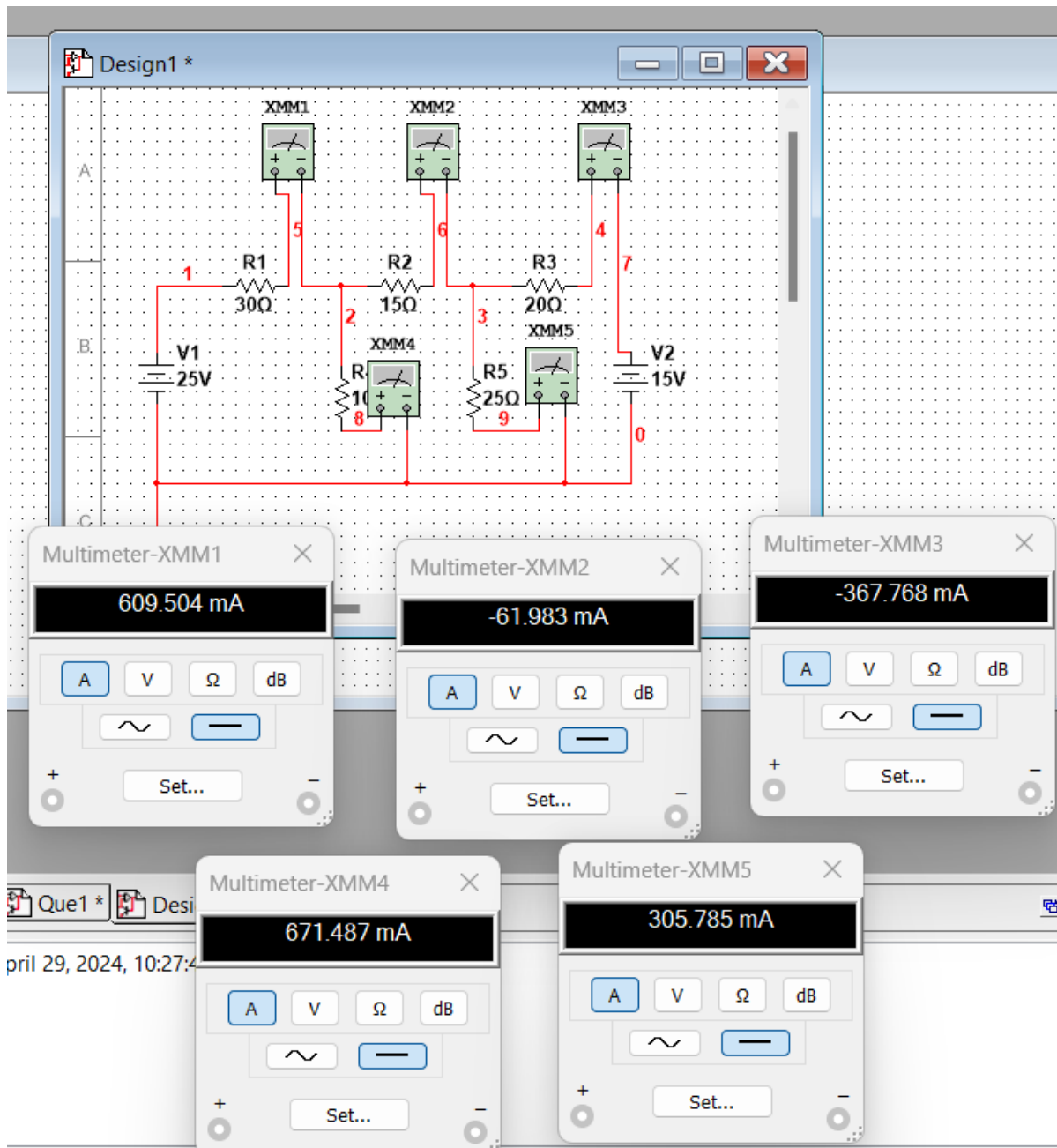The results of simulation are as follows:



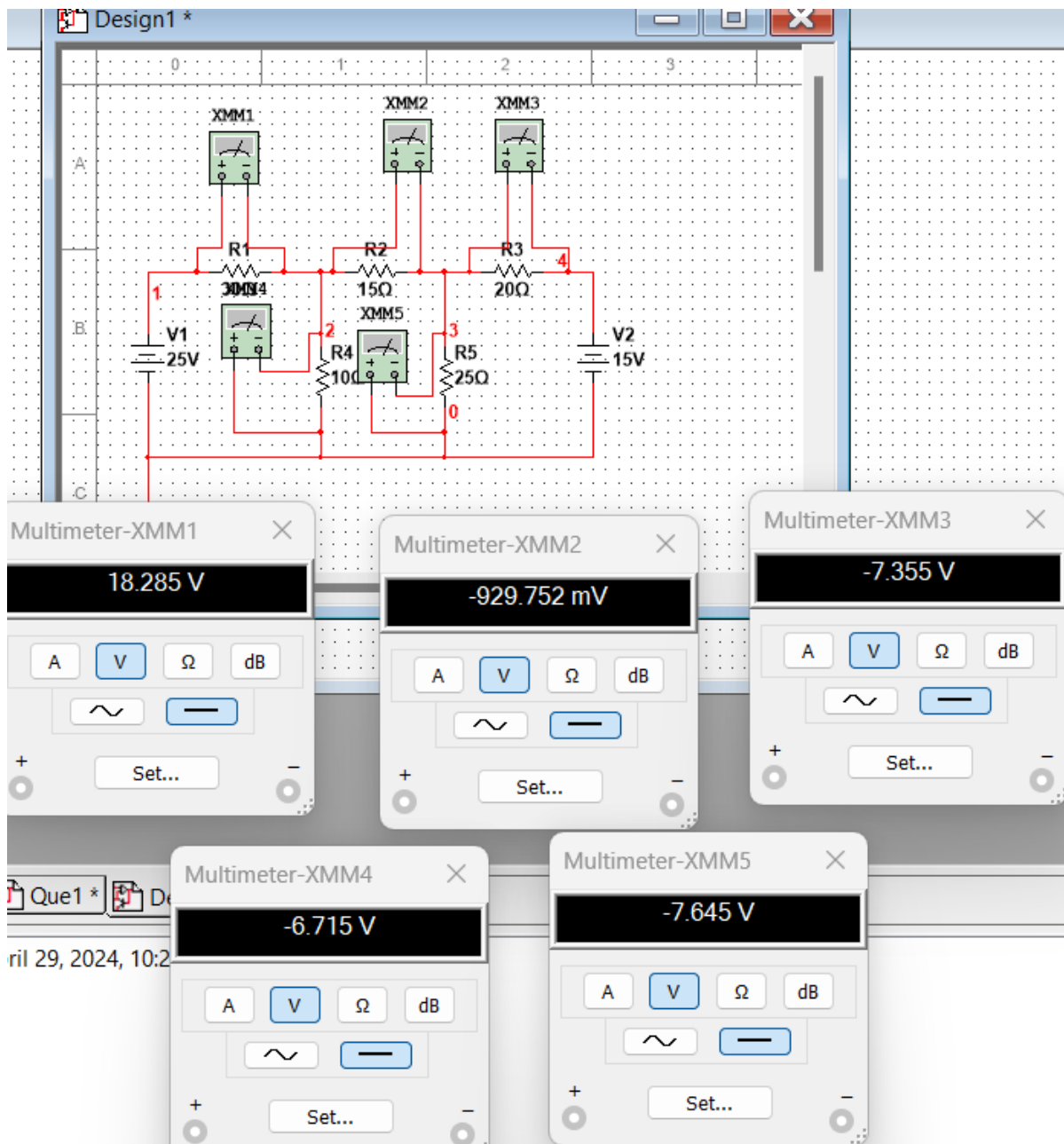

Summery

Resistor	R1	R2	R3	R4	R5
Calculated Voltage Drop	18.2851 V	-0.9297 V	-7.3554 V	-6.7149 V	7.6446 V
Calculated Current	609.5 mA	-62.0 mA	-367.8 mA	671.5 mA	305.8 A
Simulated Voltage Drop	18.285 V	-0.930 V	-7.355 V	-6.715 V	-7.645 V
Simulated Current	609.504 mA	-61.983 mA	-367.768 mA	671.487 mA	305.785 mA

The simulated result fits the calculation well.

Q2

Consider the following circuit. A capacitor with $C = 0.25 \mu\text{F}$ is in series with two resistors $R_1 = 1500 \text{ k}\Omega$ and $R_2 = 3500 \text{ k}\Omega$. The RMS value of the AC voltage supplied to the circuit is 100 VAC and the frequency is 50 Hz .

Q2-1

The amplitude is $100\text{V} \times \sqrt{2} = 100\sqrt{2} = 141.4\text{V}$

$$Z = \sqrt{(R_1 + R_2)^2 + X_C^2} \text{ where } X_C = \frac{1}{2\pi fC} = 12.7\text{k}\Omega$$

$$\text{Hence, } Z = 5000.02\text{k}\Omega$$

$$I_{max} = \frac{V_{max}}{Z} = 28.2\mu\text{A}$$

$$V_{max,R_1} = R_1 I_{max} = 42.3\text{V}$$

$$V_{max,R_2} = R_2 I_{max} = 98.7\text{V}$$

$$V_{max,X_C} = X_C I_{max} = 0.36\text{V}$$

For resistors, the phase angle between the current and the voltage is 0° , so $\Phi_{R_1} = \Phi_{R_2} = 0$; for capacitor, $I = \frac{dQ(t)}{dt} = \frac{CdV(t)}{dt} = C \frac{dV_{max}\sin(\omega t)}{dt} = CV_{max}\sin(\omega t + \frac{\pi}{2})$

So the phase angle of the capacitor is $\Phi_{C_2} = 0$

Q2-2

$$Z = 5000.02\text{k}\omega$$

$$\phi = \tan^{-1} \frac{V_{max,X_C}}{V_{max,R_1} + V_{max,R_2}} = 0.146^\circ$$


Q2-3

The circuit is run in the multisim.


Simulation of Q2-1

The voltage of the AC power source is set as 141.4V .
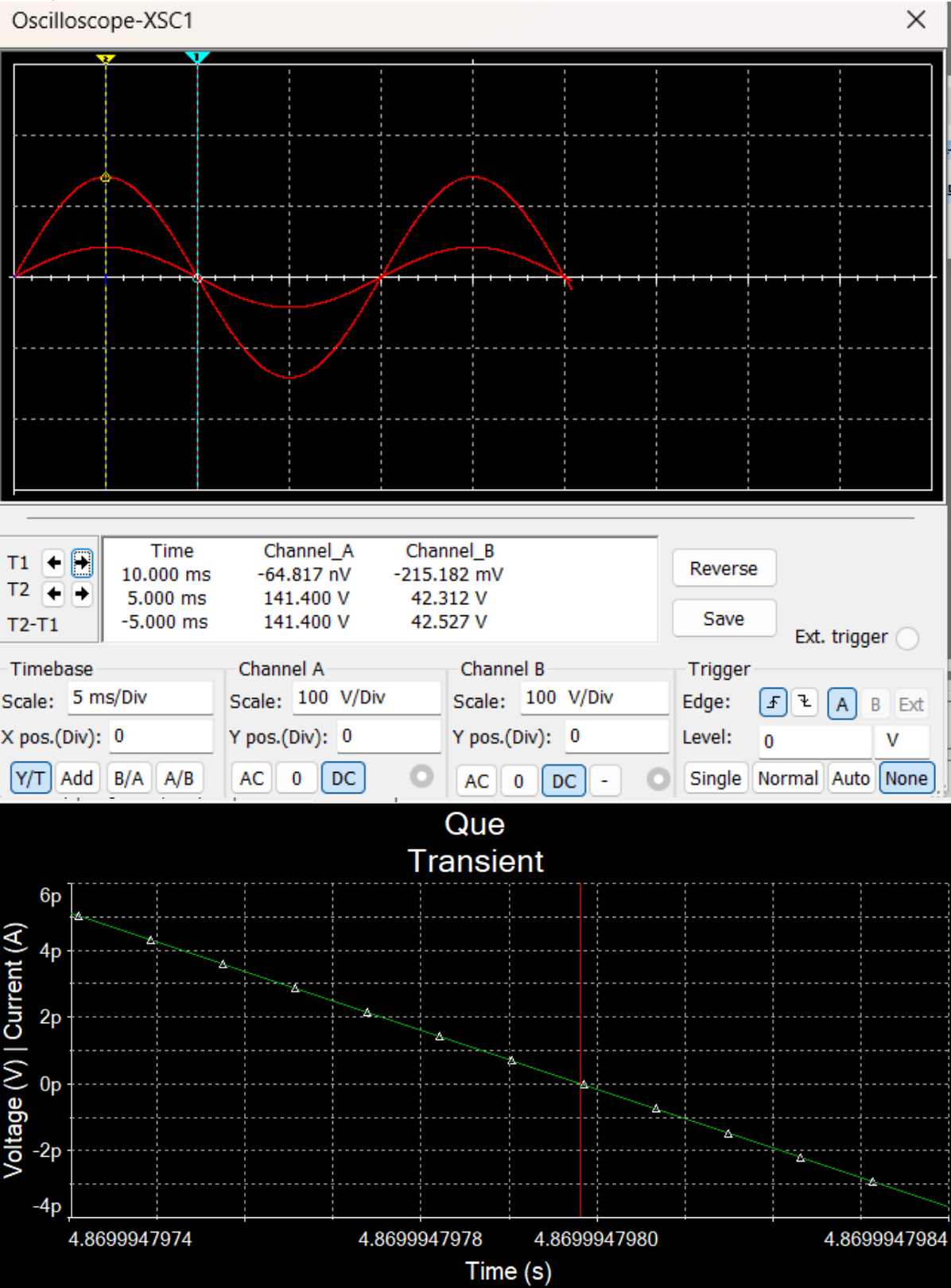
$$V_{max,R_1} = 42.312V, \text{ and } \Phi_{R_1} = 0$$



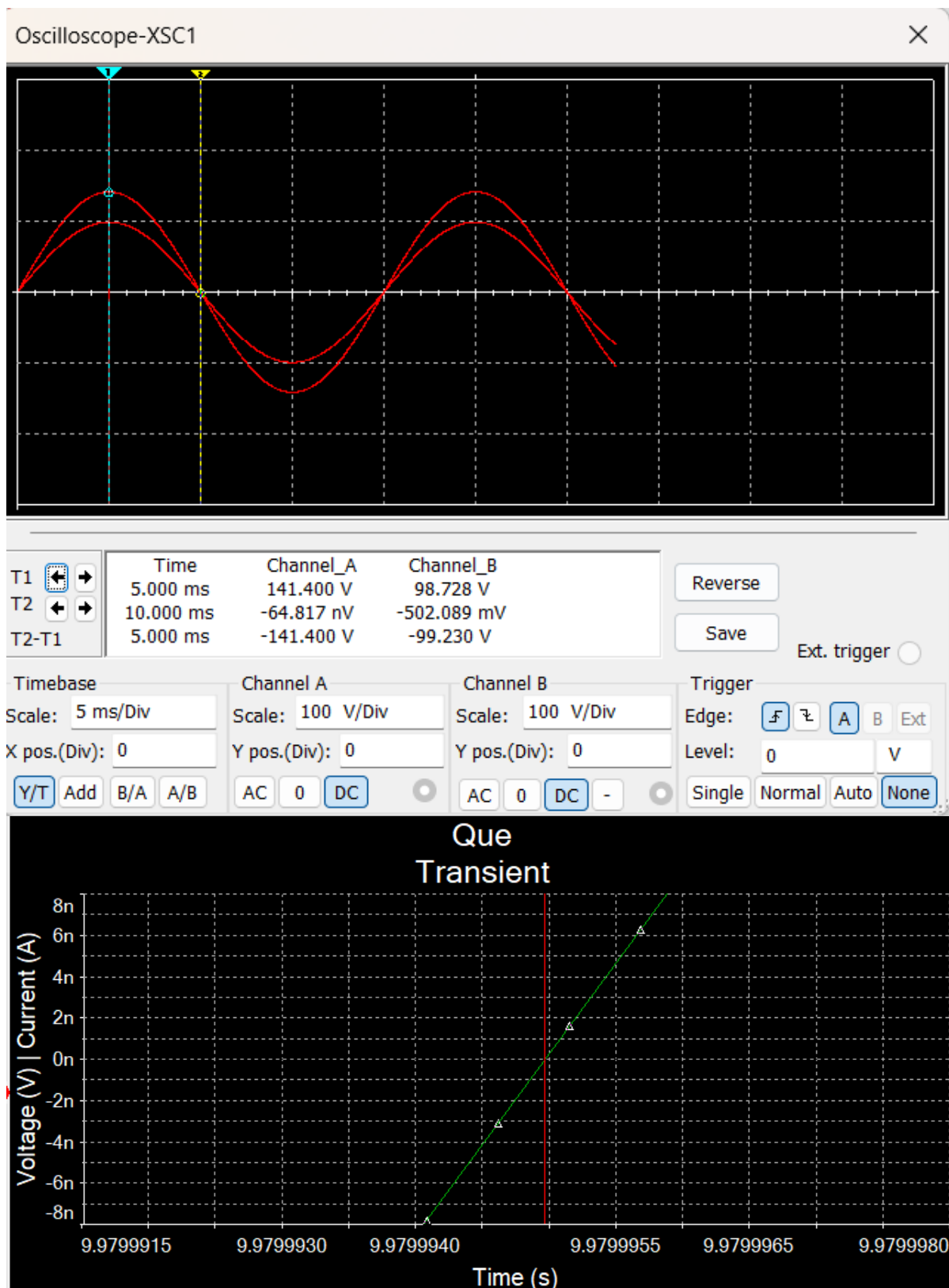
$$V_{max,R_2} = 98.728V, \text{ and } \Phi_{R_2} = 0$$



$$V_{max, X_C} = 0.356V$$

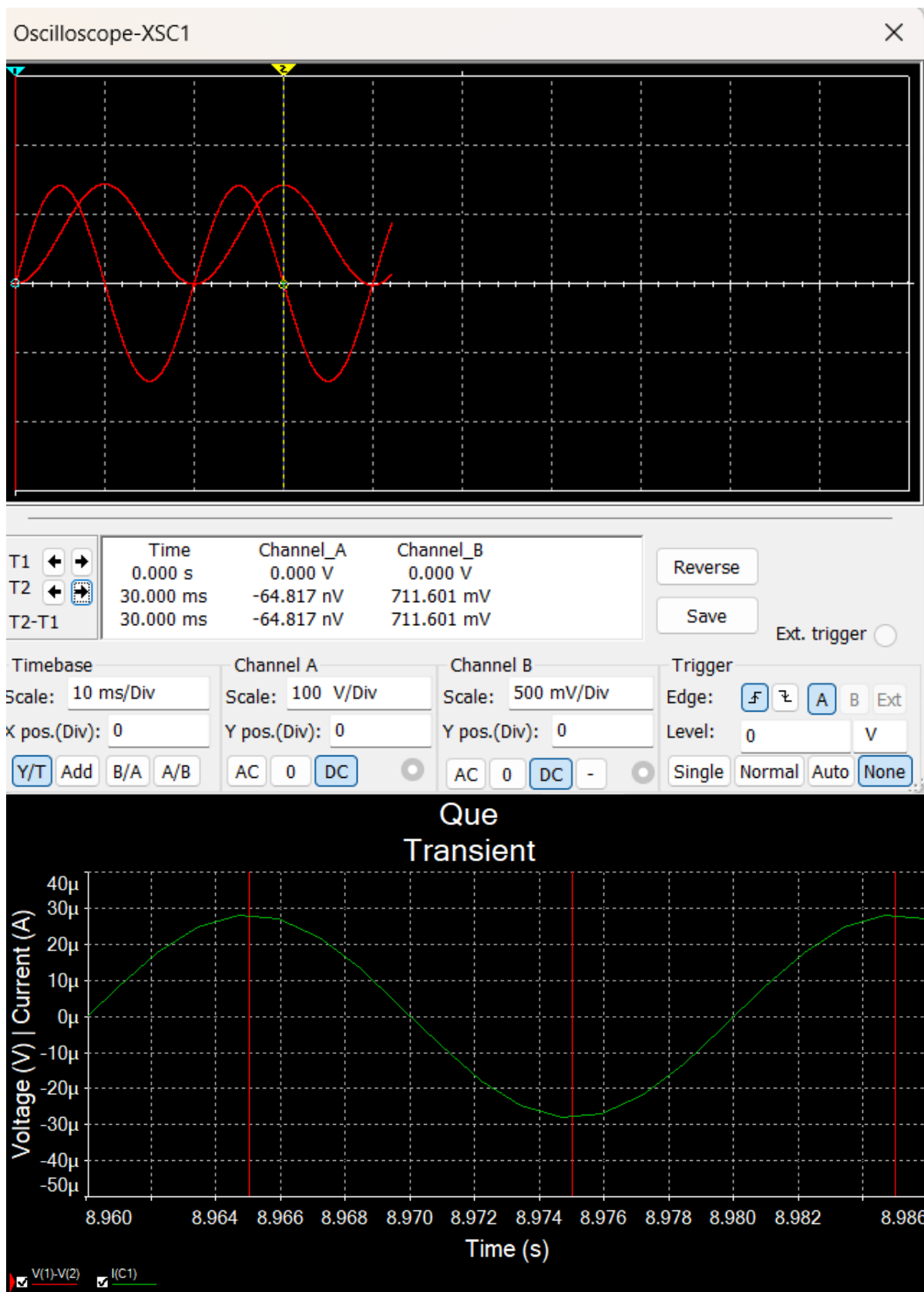(Notive that the actual voltage should be divided by 2), and $\Phi_{X_C} = 90^\circ$.




$$I_{max} = 28\mu A$$

Resistor	R1	R2	C1
Calculated Phase Drop	0°	0°	90°
Calculated V_{max}	42.3 V	98.7 V	0.36 V
Calculated I_{max}	42.3 V	98.7 V	0.36 V

Resistor	R1	R2	C1
Simulated Phase Drop	0°	0°	90°
Simulated V_{max}	42.312 V	98.728 V	0.356 V

Calculated Current	Simulated Current
$28.2\mu A$	$28\mu A$

Simulation of Q2-2

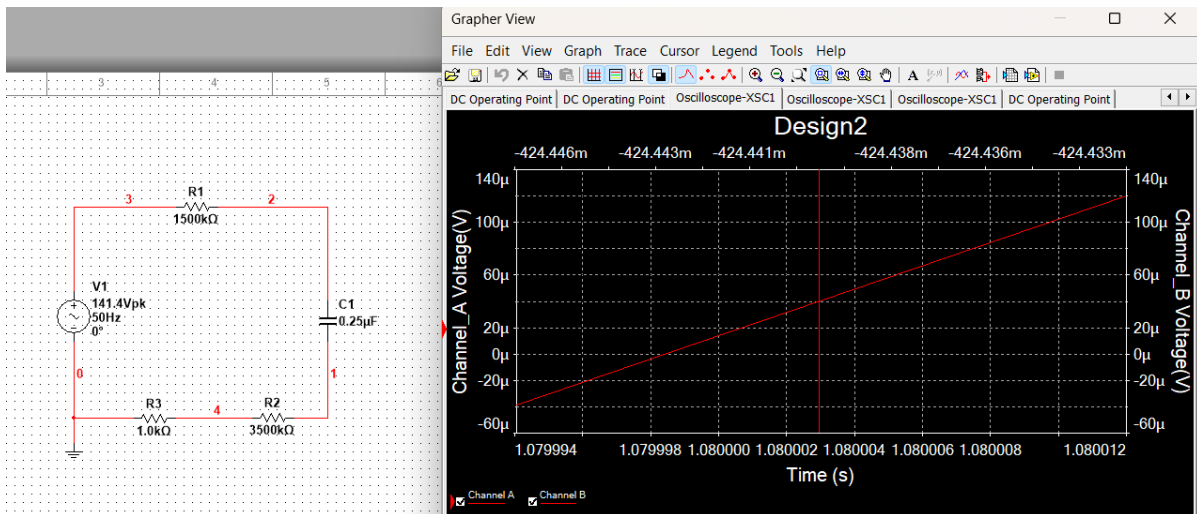

By adding a testing resistor, the time lag is $4.5 \times 10^{-6}s$, and the phase difference is 0.081° .

Q2-4

All phase shift are ignorable. The theorical phase shift is as followed.

Capacitance	Calculated phase shift	Simulated phase shift
$0.1\mu F$	0.3647°	0.365°
$0.2\mu F$	0.1823°	0.182°
$0.3\mu F$	0.1215°	0.122°
$0.4\mu F$	0.0911°	0.091°
$0.5\mu F$	0.1729°	0.173°
$0.6\mu F$	0.0607°	0.061°
$0.7\mu F$	0.0521°	0.052°
$0.8\mu F$	0.0455°	0.045°
$0.9\mu F$	0.0405°	0.040°
$1.0\mu F$	0.0364°	0.036°

Q2-5


All phase shift are ignorable. The theorical phase shift is as followed.

freq	Calculated phase shift	Simulated phase shift
50Hz	0.1459°	0.146°
100Hz	0.0729°	0.073°
150Hz	0.0486°	0.049°
200Hz	0.0364°	0.036°
250Hz	0.0291°	0.029°
300Hz	0.0243°	0.024°
350Hz	0.0208°	0.021°
400Hz	0.0182°	0.018°
450Hz	0.0162°	0.016°
500Hz	0.0145°	0.014°


As shown above, when the frequency raise, the phase difference decreased.

Q3

The circuit in Multisim is as followed:

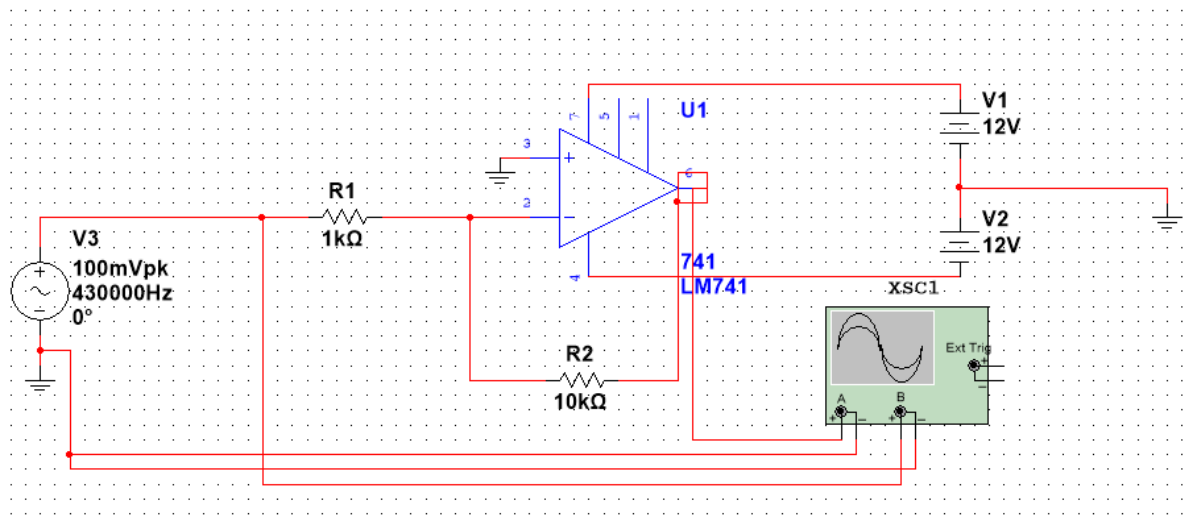


Q3-1

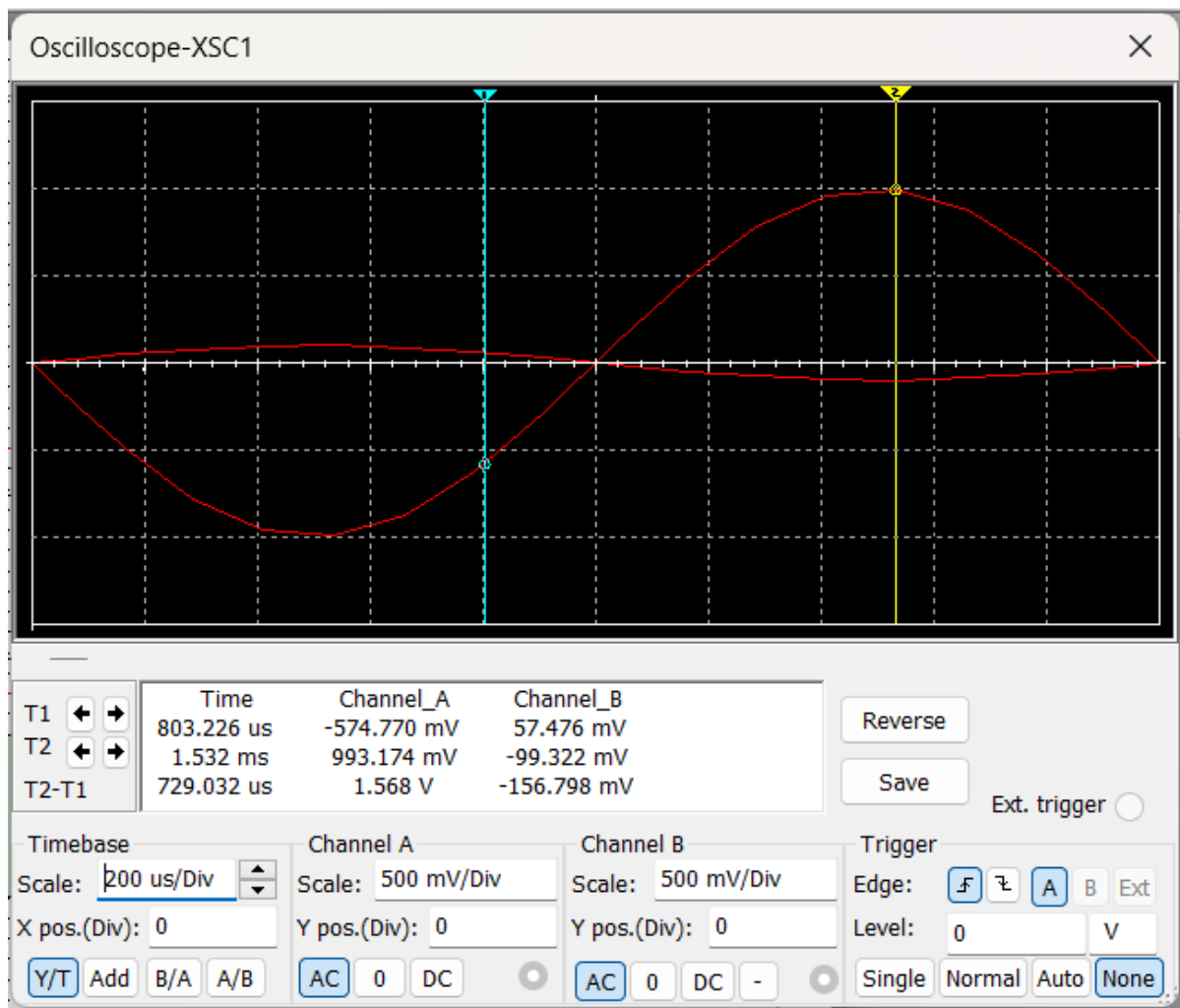

The output voltage is close to 1000 mV, and the voltage gain is $10 \log_{10} \left(\frac{1000 \text{ mV}}{100 \text{ mV}} \right) = 10$

Q3-2

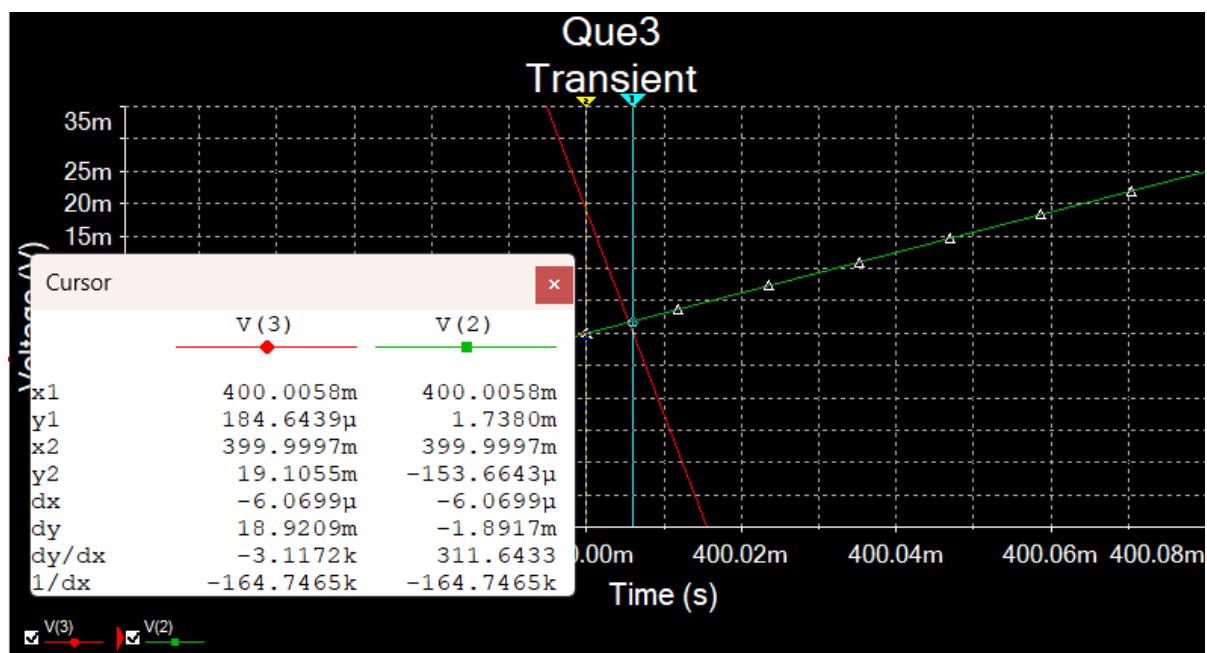

The phase difference is $2\pi \times \frac{(400.0058 \text{ ms} - 399.9997 \text{ ms})}{2 \text{ ms}} = 0.01916 \text{ rad}$

Q3-3

freq	Voltage gain	GBPW
$10^2 Hz$	$10.051 dB$	N/A
$10^3 Hz$	$10.051 dB$	N/A
$10^4 Hz$	$10.025 dB$	N/A
$5 \times 10^4 Hz$	$9.44 dB$	472000
$10^5 Hz$	$8.073 dB$	807300
$5 \times 10^5 Hz$	$2.0951 dB$	1047550
$8.6 \times 10^5 Hz$	$1 dB$	860000

From the results above, when the frequency increase, the voltage gain first remains unchanged until the freq reaches about $5 \times 10^4 Hz$, and the frequency decrease, and the gain-bandwidth product (GBPW) is around 9×10^5 .

Q3-4

the bandwidth at $A = 10$ is $4.3 \times 10^5 Hz$

Q4

Q4-1

Since the ideal voltage gain is $A_{1/2/3} = -\frac{R_F}{R_{1/2/3}}$, the output should be $V_{out} = -\frac{R_F}{R_1} V_1 - \frac{R_F}{R_2} V_2 - \frac{R_F}{R_3} V_3$. The requirements is $V_{out} = -5V_1 - 2V_2 - 0.1V_3$.

Hence, the ratio is: $R_f : R_1 : R_2 : R_3 = 0.2 : 0.5 : 10 : 1$

If $R_f = 100k\Omega$, $R_1 = 20k\Omega$, $R_2 = 50k\Omega$, $R_3 = 1M\Omega$

Q4-2

Since $V_1 = 100V_{DC}$, $V_2 = -5V_{DC}$, $V_3 = 4\sin(2\pi ft)V = 4\sin(100\pi t)V$,
 $V_{out} = -500 + 10 - 0.4\sin(100\pi t) = -490 - 0.4\sin(100\pi t)$.

The theoretical minimum and maximum value are $-490.4V$ and $-489.6V$. The $V - t$ diagram by Microsoft Calculator is as followed:



The detected minimum and maximum value are $-490.374V$ and $489.590V$. The result is as followed:

